



555IC

All changes saved



Simulator time: 00:00:23

Code

Stop Simulation

Send To



Components

Basic

Search



Resistor



LED



Pushbutton



Potentiometer



Capacitor



Slideswitch



9V Battery



Coin Cell 3V  
Battery



1.5V Battery




Breadboard  
Small




micro:bit



Arduino Uno  
R3

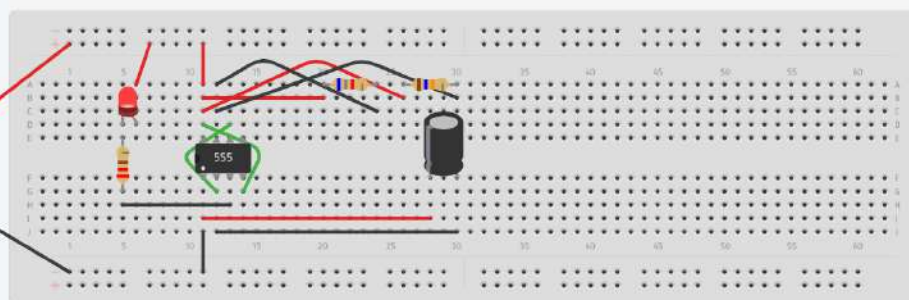

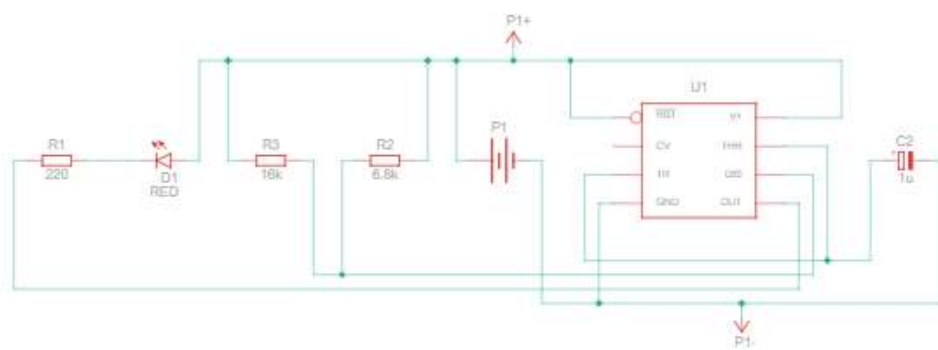

Name	Quantity	Component
P1	1	6.3 , 5 Power Supply
U1	1	Timer
D1	1	Red LED
R1	1	220 $\Omega$ Resistor
R2	1	6.8 k $\Omega$ Resistor
R3	1	16 k $\Omega$ Resistor
C2	1	10 $\mu$ F, 16 V Polarized Capacitor

